



Kasarani Campus
Off Thika Road
Tel. 2042692 / 3
P. O. Box 49274, 00100
NAIROBI
Westlands Campus
Pamstech House
Woodvale Grove
Tel. 4442212
Fax: 4444175

KIRIRI WOMENS' UNIVERSITY OF SCIENCE AND TECHNOLOGY
UNIVERSITY EXAMINATION, 2016/2017 ACADEMIC YEAR
FIRST YEAR, FIRST SEMESTER EXAMINATION
FOR THE DEGREE OF BACHELOR OF SCIENCE
(COMPUTER SCIENCE)

Date: 10th August, 2016.

Time: 11.00am –1.00pm

KCS 206 - DIGITAL LOGIC AND DESIGN

INSTRUCTIONS TO CANDIDATES

ANSWER QUESTION ONE (COMPULSORY) AND ANY OTHER TWO QUESTIONS

QUESTION ONE (30 MARKS)

- a) Perform the Boolean algebra simplification. $\bar{A}BC + A\bar{B}C + AB\bar{C} + ABC$ (7 Marks)
- b) Why do you need to know about Karnaugh maps? (2 Marks)
- c) What is the basic difference between Latches and Flip flops? (2 Marks)
- d) With help of diagrams use NOR gate to make NOT, AND, NAND and OR gates. (8 Marks)
- e) With the help of a diagram explain edge triggered Flip-Flop. (6 Marks)
- f) Convert the following;
- i) $(247.6815)_{10} = ()_8$
- ii) $(175.3942)_{10} = ()_{16}$ (5 Marks)

QUESTION TWO (20 MARKS)

- a) Simplify each Boolean expression to one of the following ten expressions;
- i) $A(A + \bar{A}) + B = AA + A\bar{A} + B$ (2 Marks)
- ii) $(A+B)(\bar{A}+B)\bar{B} = (A+B)(\bar{A}\bar{B} + B\bar{B})$ (3 Marks)
- iii) $(\overline{AB + \bar{B}})(\overline{B + \bar{A}B}) = 0$ (2 Marks)
- iv) $\overline{\overline{A + B}} =$ (3 Marks)

- b) With a neat diagram explains full subtractor with truth table? (5 Marks)
- c) Illustrates the distributive law in terms of gate implementation. (5 Marks)

QUESTION THREE (20 MARKS)

- a) With help of a diagram explain D-type positive-edge triggered flip-flop. (6 Marks)
- b) With diagrams, truth table proof 10,11 and 12 Basic rules of Boolean algebra. (14 Marks)

QUESTION FOUR (20 MARKS)

- a) State and explain both De-Morgans theorems (6 Marks)
- b) Explain in details “Don’t Care” Conditions in k-map (6 Marks)
- c) Using Boolean algebra techniques, simplify this expression $AB + A(B + C) + B(B + C)$ (5 Marks)
- d) For the above question (c) simplifies using gates (3 Marks)

QUESTION FIVE (20 MARKS)

- a) Discuss variable, complement, and literal terms as used in Boolean algebra. (4Marks)
- b) Define the following terms; (6 Marks)
- i) Bit
 - ii) Byte
 - iii) Nibble
 - iv) Word
- c) Simplify: $A(A + B) + (B + AA)(A + B)$ (4 Marks)
- d) What is a race around condition related to JK Flip Flop? (6 Marks)