



Kasarani Campus

Off Thika Road
Tel. 2042692 / 3

P.

O. Box 49274, 00100

NAIROBI

Westlands Campus
Pamstech House
Woodvale Grove
Tel. 4442212
Fax: 4444175

**KIRIRI WOMEN'S UNIVERSITY OF SCIENCE AND TECHNOLOGY
UNIVERSITY EXAMINATION, 2023/2024 ACADEMIC YEAR
SECOND/THIRD YEAR, FIRST/SECOND SEMESTER EXAMINATION
FOR THE BACHELOR OF SCIENCE IN COMPUTER SCIENCE
KCS 206 – DIGITAL LOGIC AND DESIGN**

Date: 09TH AUGUST 2023

Time: 8:30AM – 10:30AM

INSTRUCTIONS TO CANDIDATES

ANSWER QUESTION ONE (COMPULSORY) AND ANY OTHER TWO QUESTIONS

QUESTION ONE (30 MARKS)

- a) Express the following Boolean expression in canonical form sum of products notation and draw a truth table. (6 Marks)

$$f(a, b, c) = \bar{a}. \bar{b}. c + \bar{a}. b. c + \bar{a}. \bar{b}. \bar{c} + \bar{a}. b. \bar{c}$$

- b) A computer manipulates information in digital form or more precisely, binary form. Explain (4 Marks)
- c) Draw a system diagram and generate a truth table for the function, $f(x, y, z) = x.y + y.z + \bar{z}.y$. (6 Marks)
- d) Explain difference between one's complement and two's complement as used in subtraction operations in digital computers. (4 Marks)
- e) Write the 2's complement for each of the following 5-bit binary numbers.
- i) 01001
 - ii) 01011
 - iii) 00111 (6 Marks)
- f) Define the following (4 Marks)
- i) Latches
 - ii) Flip-flops

QUESTION TWO (20 MARKS)

- a) State and explain any three advantages of digital system over analog systems. (6 Marks)
- b) Explain the meaning of product of sums(POS) and sum of products(SOP). (4 Marks)

- c) Using the truth table below, show the SOP expression and then minimize it using a K-map and draw the minimized circuit. (10 Marks)

x	y	z	f
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

QUESTIONS THREE (20 MARKS)


- a) Convert the following numbers into their equivalent binary number. (4 Marks)
- i) 227_{10} (4 Marks)
- ii) 27.125_{10} (3 Marks)
- iii) $8B3_{16}$ (3 Marks)
- b) A digital circuit has three inputs **A**, **B** and **C**. Inputs **A** and **B** are applied to an **OR** gate. The output of the gate is applied to one input of **AND** gate. Input **C** is passed through a **NOT** gate before being applied to the other input of the **AND** gate. Draw the logic diagram and show the output expression of the **AND** gate. (6 Marks)
- c) Develop a truth table for the logic diagram in b above. (4 Marks)

QUESTION FOUR (20 MARKS)

- a) Sequential circuits are classified into two types, with the help of a well labelled diagram, explain each one of them. (8 Marks)
- b) What is the main difference between Static RAM (SRAM) and Dynamic RAM (DRAM). (2 Marks)
- c) Simplify and draw a logic diagram for the following Boolean expression.
- i) $A + A \bar{B} = A + B$
- ii) $(A + B)(A + C) = A + BC$ (10 Marks)

QUESTION FIVE (20 MARKS)

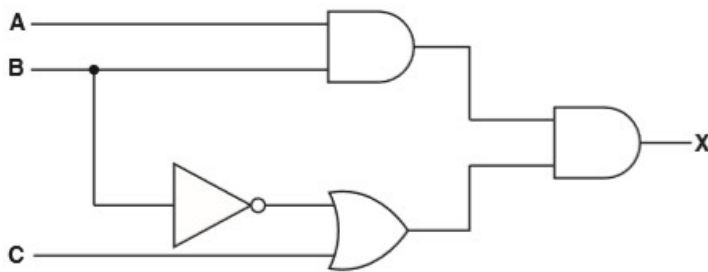- a) Explain the following terminologies as used in K-Maps methodology for minimizing logical expressions.
- i) An implicant
 - ii) A prime implicant (4 Marks)
- b) Briefly explain the difference between min- terms and max-terms as used in canonical and standard form of functions. (4 Marks)
- c) Describe four differences between flip-flops and latches (4 Marks)
- d) The following figure shows a logic circuit diagram.



- i) Write logic expressed for the above circuit. (4 Marks)
- ii) Prepare truth table. (4 Marks)